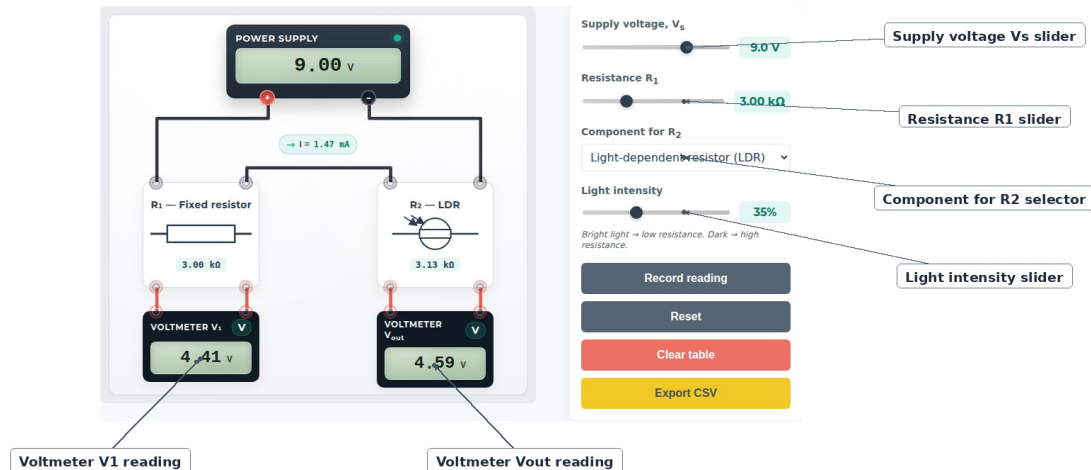


Investigating Potential Dividers

Resistance Ratio, LDR and Thermistor Circuits

Aim:

You are investigating how a potential divider splits voltage between two resistors.



Prediction:

Set $R_1 = R_2 = 1000 \, \Omega$. Before you read the voltmeters, predict what V_1 and V_{out} will each read if $V_s = 6.0 \, \text{V}$.

V_1 : V V_{out} : V

Test it in the sim.

Method:

1. Set the Supply voltage, V_s to 6.0 V. Leave the Component for R_2 as Fixed resistor, and set Resistance R_1 and Resistance R_2 both to 1000 Ω .
2. Click Record reading. Note V_1 , V_{out} and the current shown above the resistors.
3. Increase R_1 to 5000 Ω while keeping R_2 at 1000 Ω , then click Record reading again.
4. Set R_1 back to 1000 Ω and increase R_2 to 5000 Ω instead, then click Record reading again.
5. Choose two more R_1/R_2 combinations of your own, spread across the slider range, and record a reading for each.
6. Change the Component for R_2 to Light-dependent resistor (LDR). Set the Light intensity slider close to 100% (bright) and record a reading, then close to 0% (dark) and record another.
7. Change the Component for R_2 to Thermistor (NTC). Record a reading at a low temperature (close to 0 $^{\circ}\text{C}$) and another at a high temperature (close to 80 $^{\circ}\text{C}$).

Results:

Vs (V)	R1 (Ω)	R2 (Ω)	V1 (V)	Vout (V)	I (mA)

Analysis:

Look down your table: how does the ratio $R1 : R2$ compare with the ratio $V1 : V_{out}$ for your fixed-resistor rows? Check whether $V1 + V_{out}$ always adds up to V_s .

.....

.....

.....

Compare your two LDR readings. Explain why V_{out} changes the way it does as the light dims, linking your answer to how the LDR's resistance responds to light.

.....

.....

.....

Compare your two thermistor readings. Explain why V_{out} changes the way it does as the temperature rises, linking your answer to how the thermistor's resistance responds to temperature.

.....

.....

.....